

---


# A Systematic Approach to MOST Circuit Design and Analysis:
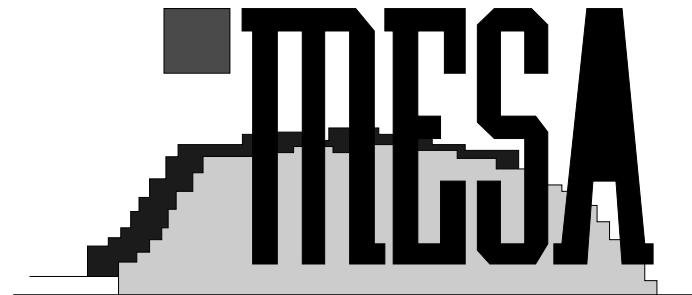
## Classification of 2VCCS Circuits

Eric A. M. Klumperink



University of Twente  
Department of Electrical Engineering  
Enschede, The Netherlands



MESA Research Institute

# **Contents**

**Introduction: Motivation and Aim**

**A Design Philosophy for MOST Circuits**

**=> PhD Thesis: “Transconductance Based CMOS Circuits”**

**A Classification System for 2VCCS Circuits**

**Application Examples**


**Conclusions**

---

## Introduction: Problem and Aim
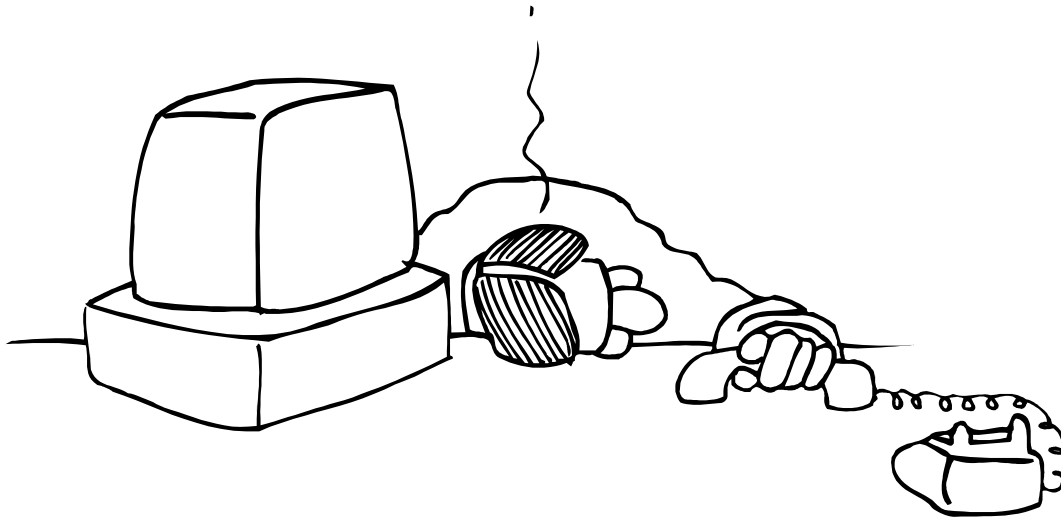
### Analog Computer Aided Design:


- Analysis well developed, e.g. simulation, symbolic analysis
- Synthesis largely intuitive, especially for *transistor topology*



**Teach intuition  
to a computer??**
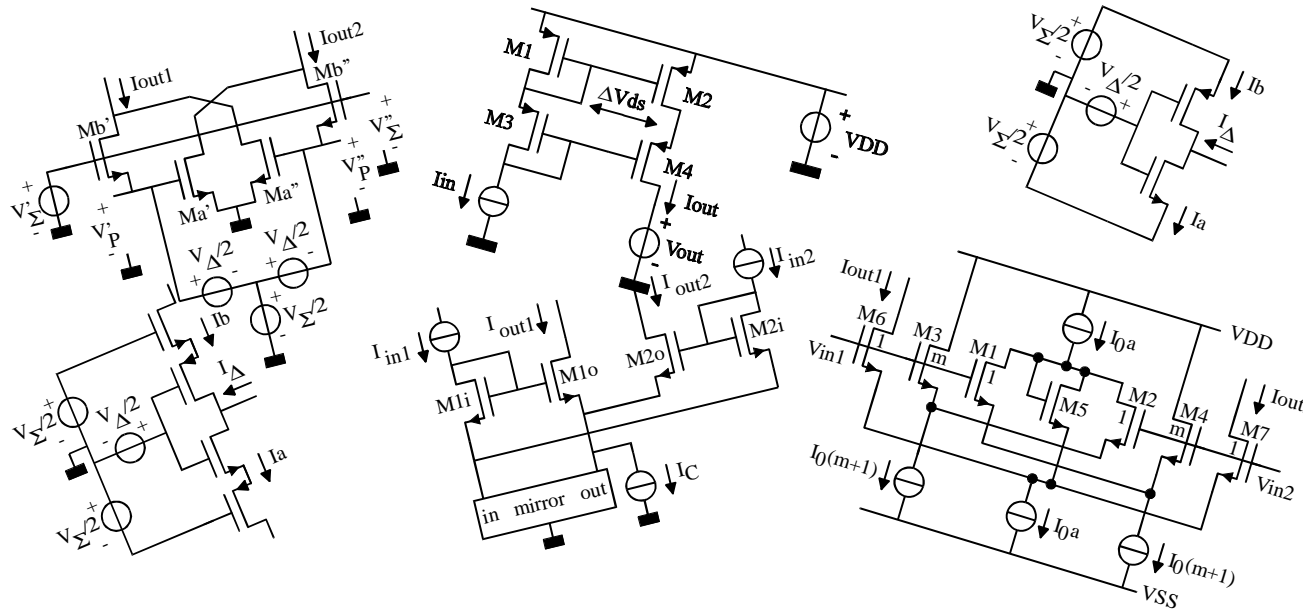
## AIM: Systematic approach

- **Literature: fragmentary, many circuit topologies!**



- **Questions: Variations on a theme? Relative merits?**

**=> Aim:** 1) *Create overview of different possible topologies*  
 2) *Predict and compare circuit performance*

## **A Design Philosophy for MOST Circuits**


**Classify on what? What is important during design?**

**MOST design experience:**

- **Combine simple basic circuits (differential pair, mirror)  
few components  $\Leftrightarrow$  HF, low noise, low current**
- **Mainly MOSTs, saturated region (current output)**
- **Transconductance  $g_m$  of MOST is crucial:**
  - **Good model up to high frequencies**
  - **Matching of transconductance is good ( $< 1\%$ )**
  - **Electronic variability (self-correction/adaptivity)**
  - **Large  $g_m$ -range: nS....S**

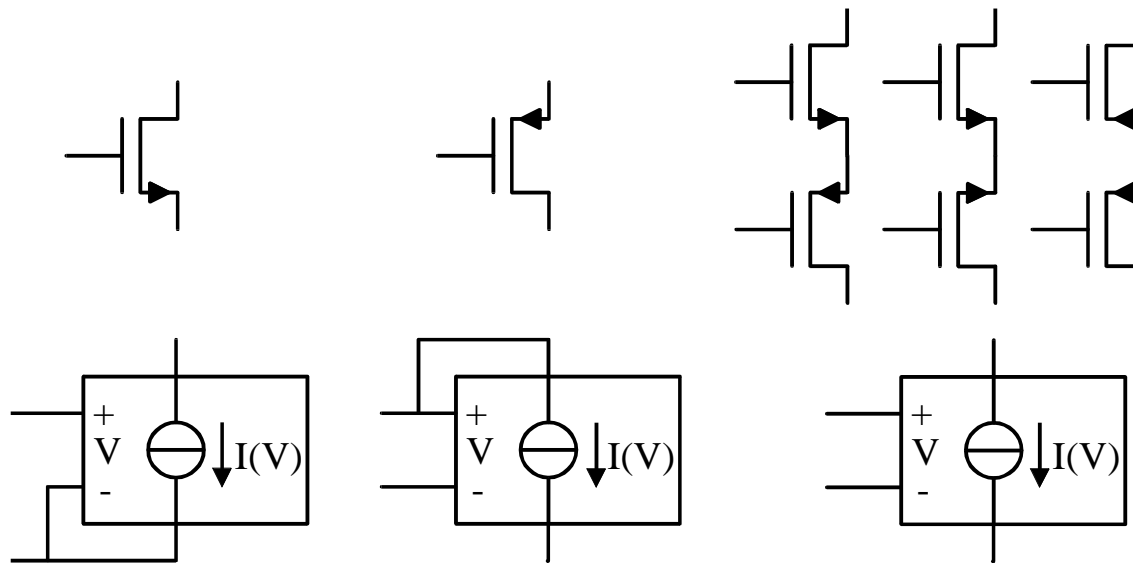
# PhD Thesis: Transconductance Based CMOS Circuits

- **MOST = Voltage Controlled Current Source (VCCS)**



- **Synthesize linear two-ports with *only* VCCSs**
  - **All two-ports with 2 VCCSs (Circuit Generation)**
- => 145 topologies, covering most needs => 2VCCS circuits**

# Classification of 2VCCS Circuits

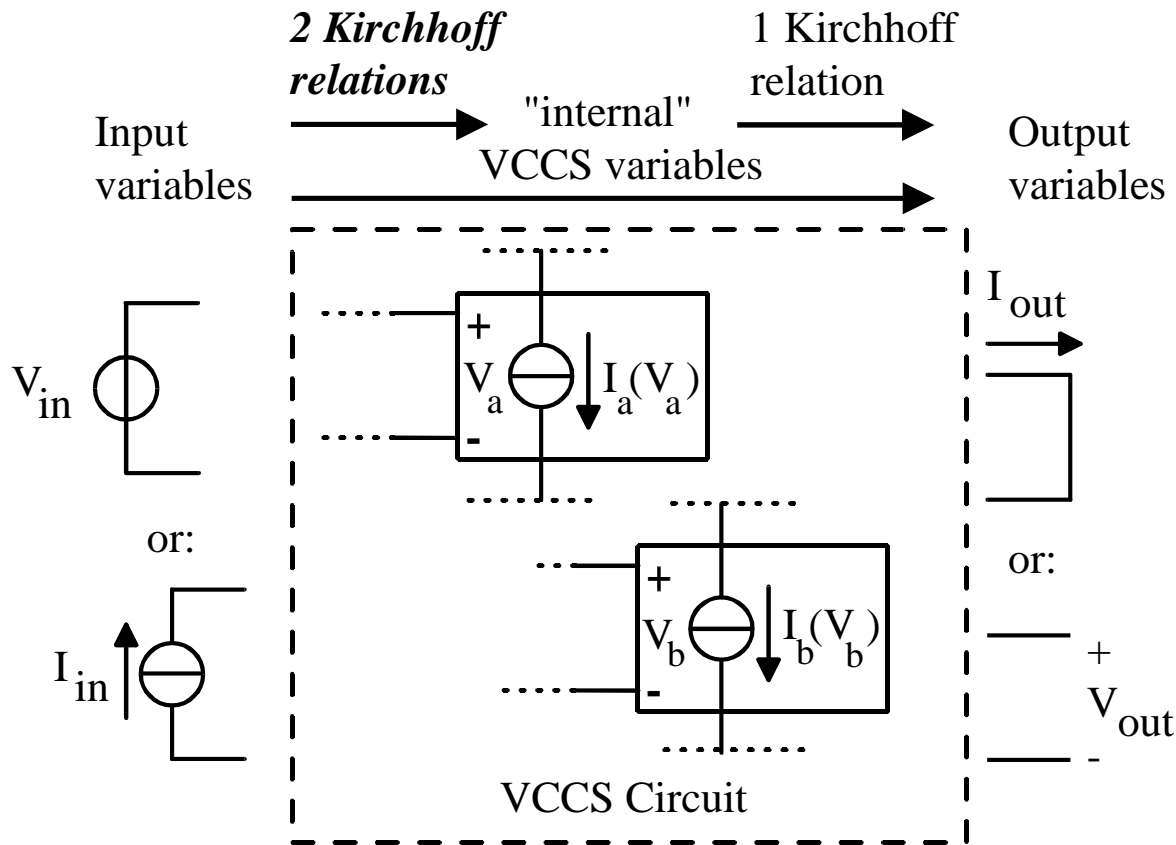

## Analyse electrical behaviour:


- Analyse two-port parameters
- VCCS variables are crucial!
- 4 eqns needed (4 VCCS vars)
- $I_a = g_a V_a$  and  $I_b = g_b V_b$  available
- 2 additional topology related KVL/KCL relations needed!

**Non-linear case: square-law and exponential  $I(V)$  also 2 eqns.**

***Set of 2 independent Kirchhoff relations needed!***

# All classes of 2VCCS Circuits

- Types of Kirchhoff relations:

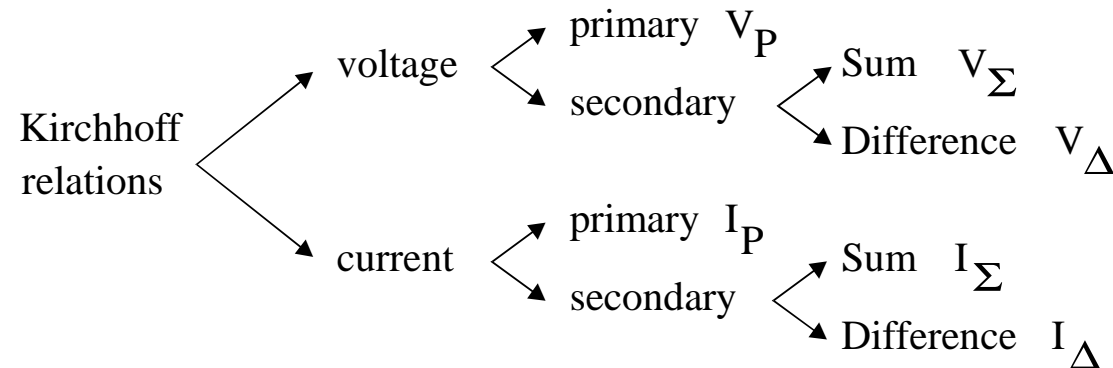





- ALL Sets of 2 relations: 3 main classes and 14 subclasses:**

$\{V, V\}$	$\{V_P, V_\Sigma\}$	$\{V, I\}$	$\{V_P, I_\Sigma\}$
	$\{V_P, V_\Delta\}$		$\{V_P, I_\Delta\}$
	$\{V_\Sigma, V_\Delta\}$		$\{V_\Sigma, I_P\}$
$\{I, I\}$	$\{I_P, I_\Sigma\}$		$\{V_\Delta, I_P\}$
	$\{I_P, I_\Delta\}$		$\{V_\Sigma, I_\Sigma\}$
	$\{I_\Sigma, I_\Delta\}$		$\{V_\Sigma, I_\Delta\}$
	$\{I_\Sigma, I_\Delta\}$		$\{V_\Delta, I_\Sigma\}$
	$\{I_\Sigma, I_\Delta\}$		$\{V_\Delta, I_\Delta\}$
	$\{I_\Sigma, I_\Delta\}$		$\{V_\Delta, I_\Delta\}$



# Application Examples

Recognise variations on a theme: 50 V-I Kernels in 4 classes
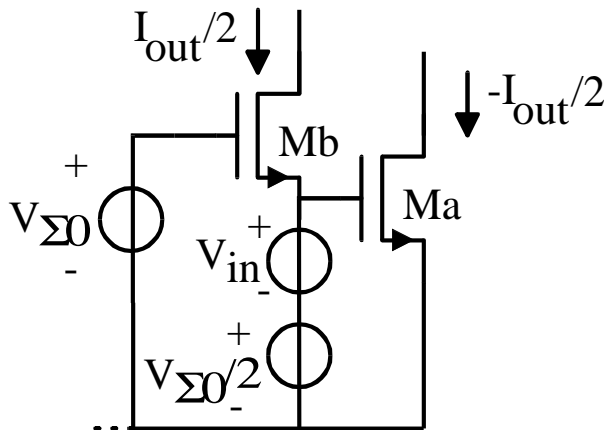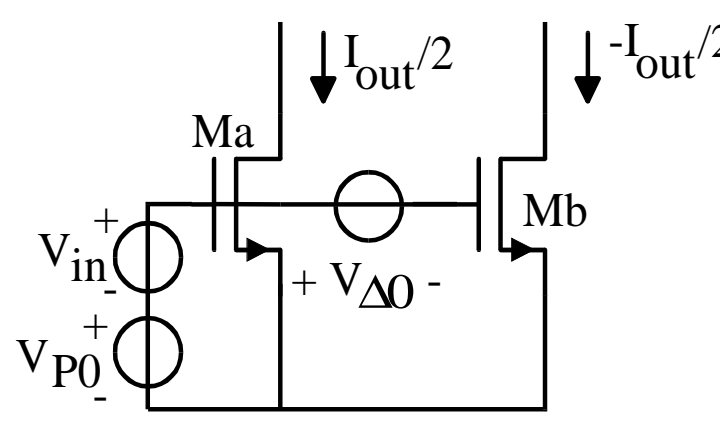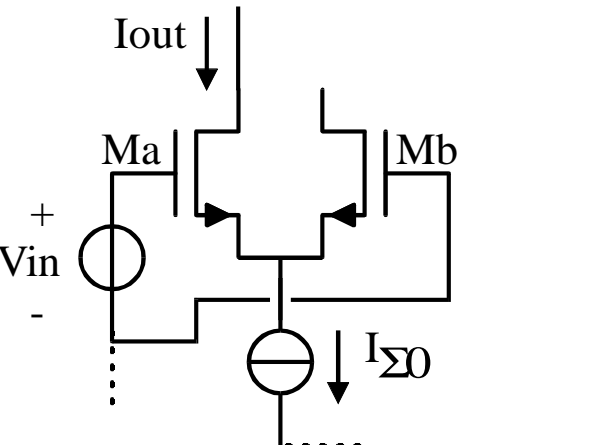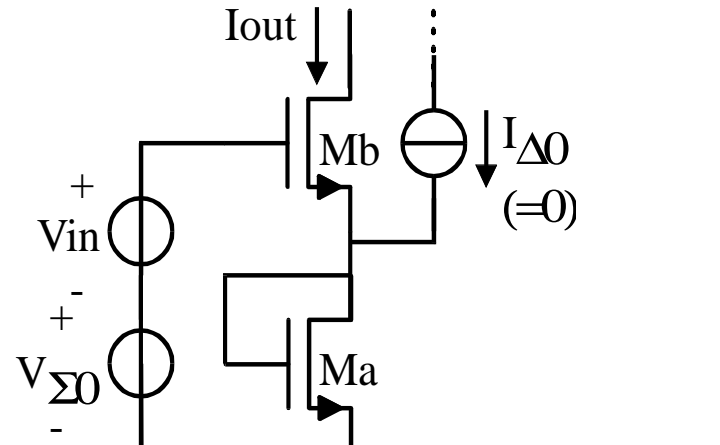
<p><math>\{V_P, V_\Sigma\}</math>, constant <math>V_\Sigma</math> (<math>&gt; 25</math> refs)</p> 	<p><math>\{V_P, V_\Delta\}</math> constant <math>V_\Delta</math> (10 refs)</p> 
<p><math>\{V_\Delta, I_\Sigma\}</math> constant <math>I_\Sigma</math> (numerous refs)</p> 	<p><math>\{V_\Sigma, I_\Delta\}</math>, constant <math>I_\Delta</math> (10 refs)</p> 

# Generating *all* Classes of V-I kernels with 2 VCCSs

Required:  $\geq 1$  KVL relation. Result: 4 really different classes

Class	Vin	1 <sup>st</sup> order coeff.Ia,Ib	2nd order coeff.Ia,Ib	3rd order coeff.Ia,Ib
$\{V_P, V_\Sigma\}$	$V_P$	$\mathbf{g_{1a}}, -\mathbf{g_{1b}}$	$\mathbf{g_{2a}}, \mathbf{g_{2b}}$	$\mathbf{g_{3a}}, -\mathbf{g_{3b}}$
	$V_\Sigma$	0, $g_{1b}$	0, $g_{2b}$	0, $g_{3b}$
$\{V_P, V_\Delta\}$	$V_P$	$\mathbf{g_{1a}}, \mathbf{g_{1b}}$	$\mathbf{g_{2a}}, \mathbf{g_{2b}}$	$\mathbf{g_{3a}}, \mathbf{g_{3b}}$
	$V_\Delta$	0, $g_{1b}$	0, $g_{2b}$	0, $g_{3b}$
$\{V_\Sigma, V_\Delta\}$	$V_\Sigma$	$\mathbf{g_{1a}/2}, \mathbf{g_{1b}/2}$	$\mathbf{g_{2a}/4}, \mathbf{g_{2b}/4}$	$\mathbf{g_{3a}/8}, \mathbf{g_{3b}/8}$
	$V_\Delta$	$\mathbf{g_{1a}/2}, -\mathbf{g_{1b}/2}$	$\mathbf{g_{2a}/4}, \mathbf{g_{2b}/4}$	$\mathbf{g_{3a}/8}, -\mathbf{g_{3b}/8}$
$\{V_\Sigma, I_P\}$	$V_\Sigma$	0, $g_{1b}$	0, $g_{2b}$	0, $g_{3b}$
$\{V_\Delta, I_P\}$	$V_\Delta$	0, $-g_{1b}$	0, $-g_{2b}$	0, $-g_{3b}$
$\{V_P, I_\Sigma\}$	$V_P$	$g_{1a}, -g_{1a}$	$g_{2a}, -g_{2a}$	$g_{3a}, -g_{3a}$
$\{V_P, I_\Delta\}$	$V_P$	$g_{1a}, g_{1a}$	$g_{2a}, g_{2b}$	$g_{3a}, g_{3b}$
$\{V_\Sigma, I_\Sigma\}$	$V_\Sigma$	no solution	no solution	no solution
$\{V_\Sigma, I_\Delta\}$ @	$V_\Sigma$	$\mathbf{g_1/2}, \mathbf{g_1/2}$	$\mathbf{g_2/4}, \mathbf{g_2/4}$	$\mathbf{g_3/8}, \mathbf{g_3/8}$
$\{V_\Delta, I_\Sigma\}$ @	$V_\Delta$	$\mathbf{g_1/2}, -\mathbf{g_1/2}$	$\mathbf{0}, \mathbf{0}$	$\mathbf{g_3/8} - (\mathbf{g_2^2/4g_1})$
$\{V_\Delta, I_\Delta\}$	$V_\Delta$	no solution	no solution	no solution

@= equal g-coefficients for VCCSa and VCCSb ; **BOLD**=different from 1VCCS

## Comparison of V-I Kernels: Figure of Merit NDR/ISS

- **DR=S/N depends on distortion and noise bandwidth NBW!**

**Assume dominant HD3:**



$$\text{HD3} \approx \frac{g_3}{4g_1} \hat{V}_{\text{in}}^2 = \left( \frac{\hat{V}_{\text{in}}}{V_{\text{IP3}}} \right)^2$$

- **Normalise: HD3 = 100% and NBW =1Hz** ( $\text{NDR} = \frac{\text{NBW}}{\text{HD3}} \text{DR}$ )
- **Figure of Merit independent of scaling:**

$$\frac{\text{NDR}}{\text{ISS}} = \frac{S}{N \cdot \text{ISS}} \Bigg|_{\substack{\text{HD3}=100\% \\ \text{NBW}=1\text{Hz}}} = \frac{\frac{1}{2} G_m V_{\text{IP3}}^2}{4 \cdot k \cdot T \cdot \text{NEF} \cdot I_{\text{SS}}}$$

***Model I(V) and noise of VCCS and analyse NDR/ISS!!!***

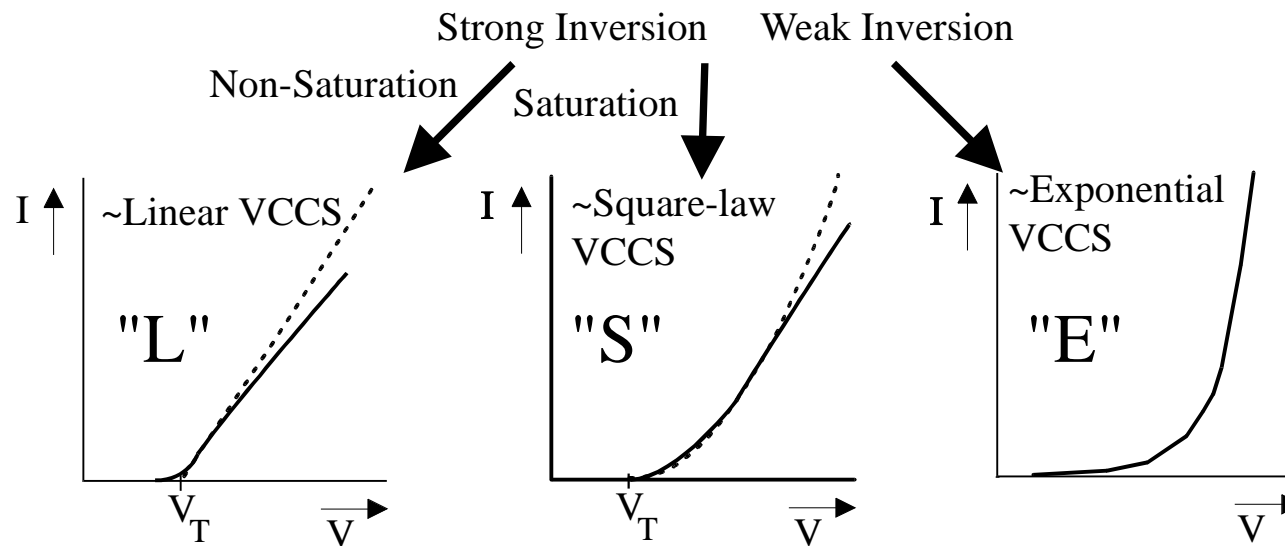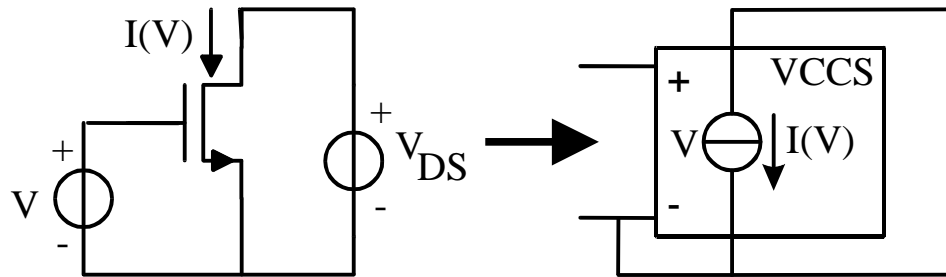
# Compare MOST V-I Kernels: 3 Operating regions




**Assume mobility reduction:**

$$\mu = \frac{\mu_o}{1 + \theta(V_{GS} - V_T)}$$
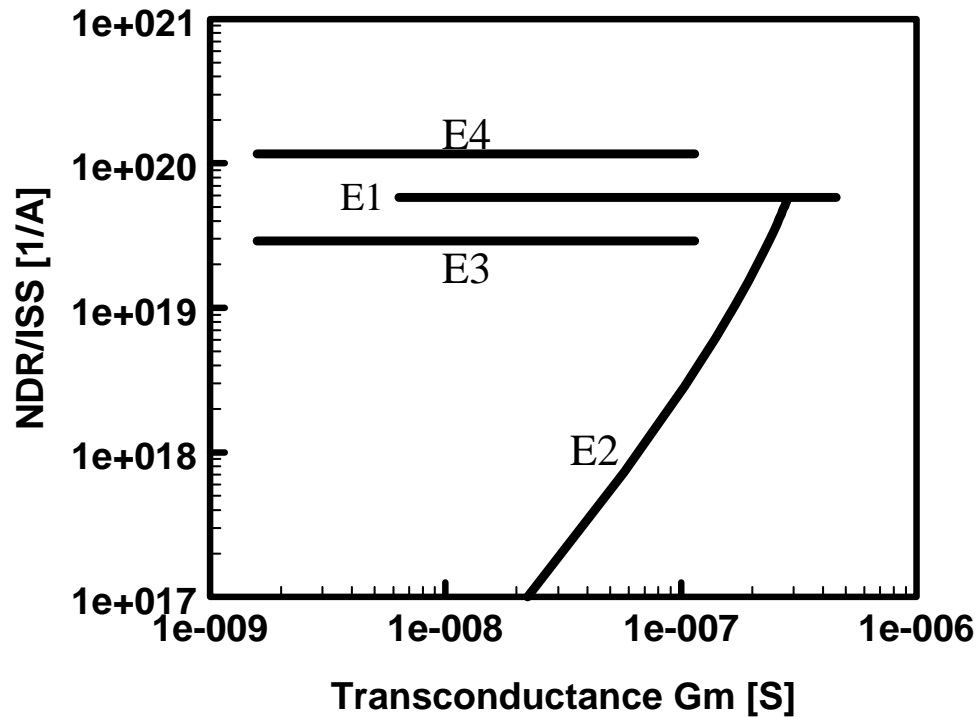
## Draw General Conclusions on Relative Merits



*Exponential cases*


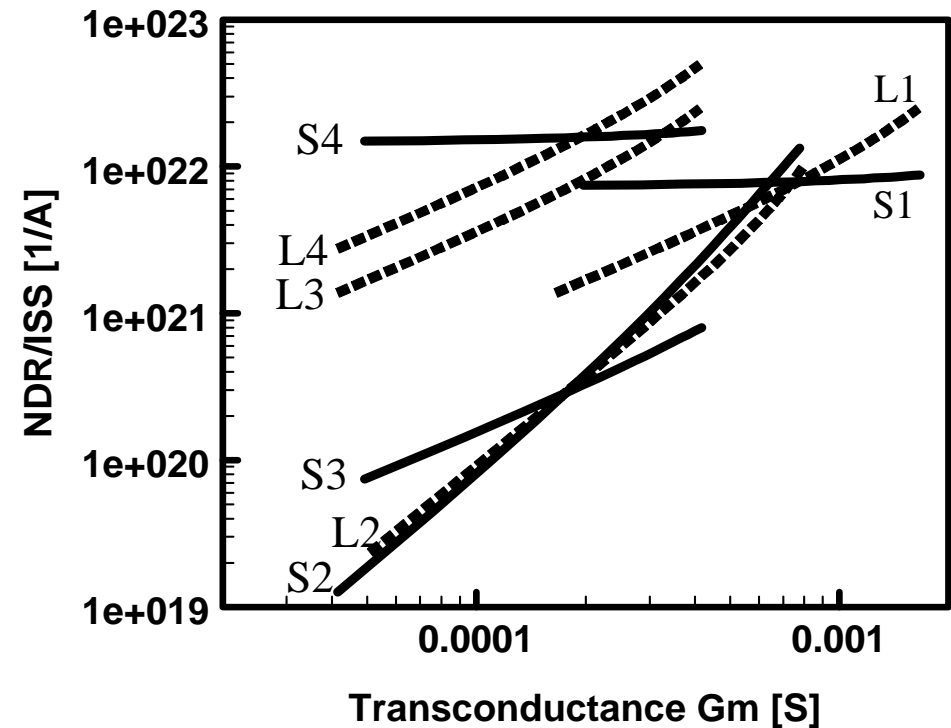


*Square-law and Linear cases;  $\theta=0.1$*

- **Exponential VCCS: worst result (different scales!)**
- **$\{V_\Sigma, I_\Delta\}$  Square-law or Linear VCCSs (S4 and L4) best!**
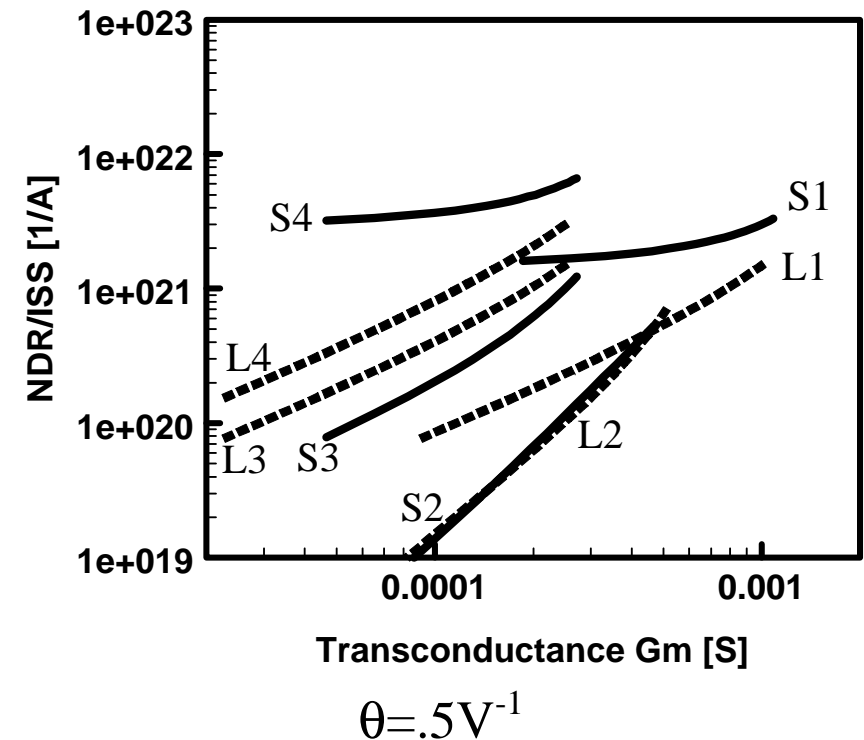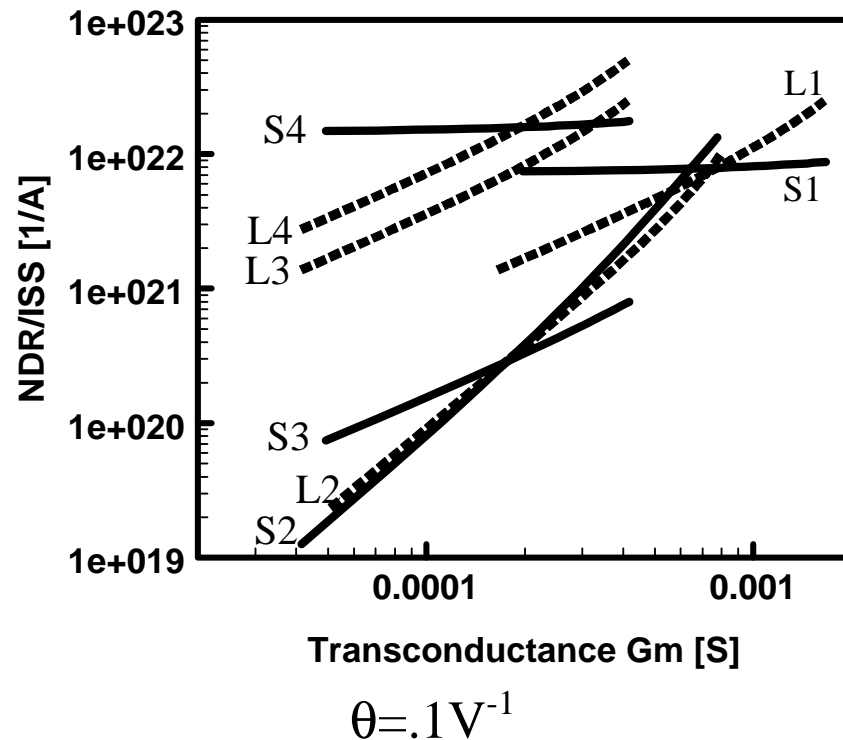
## Assess Feasibility: e.g. effect of increased $\theta$

- Results are reference for circuits design (best achievable)



- Assess feasibility, e.g. in newer technology: higher  $\theta$   
 $\Rightarrow$  worse NDR/ISS, except differential pair (S3)

---

# Conclusions

**Classification system proposed based on sets of 2 Kirchhoff relations establishing a solution for the variables of the VCCSs.**

**Usefulness shown:**

- ***Overview of all possibilities with 2 VCCSs***
- **Recognise variations on a theme: 50 Kernels, 4 classes**
- **Analyse classes of circuits in one run: general conclusions**
- **Guide designers in choosing and optimising circuits**
  - Select class with best DR/ISS
  - Use best achievable NDR/ISS as land-mark during design